

A 1GHz 0.56 pJ 4-bit Absolute-Value Detector for use in Neural Spike Sorting

**Joani Bajlozi
Sanjana Sarda**




Design Summary

- ◇ A) Circuit topology: **Optimized 3-bit Full Adder and 3-bit Comparator**
- ◇ B) Circuit Style: **Pass-Transistor Logic and Static CMOS**
- ◇ C) WHY: **Moderate Area and Fast, Regular Design**

Schematic	Layout size	Energy	Verification
$t_{p_{X0 \rightarrow OUT}} =$ 286.242 ps	X= 21 μm , Y= 19.5 μm	Sch E = 564 fJ	Func: Y
$t_{p_{X3 \rightarrow OUT}} =$ 228.465 ps	A = 409.5 μm^2	Layout E = 0.74 pJ	DRC: Y
$t_p =$ 286.242 ps	AR = 1.078		LVS: Y


Critical Path Analysis

◆ Block Diagram of Design

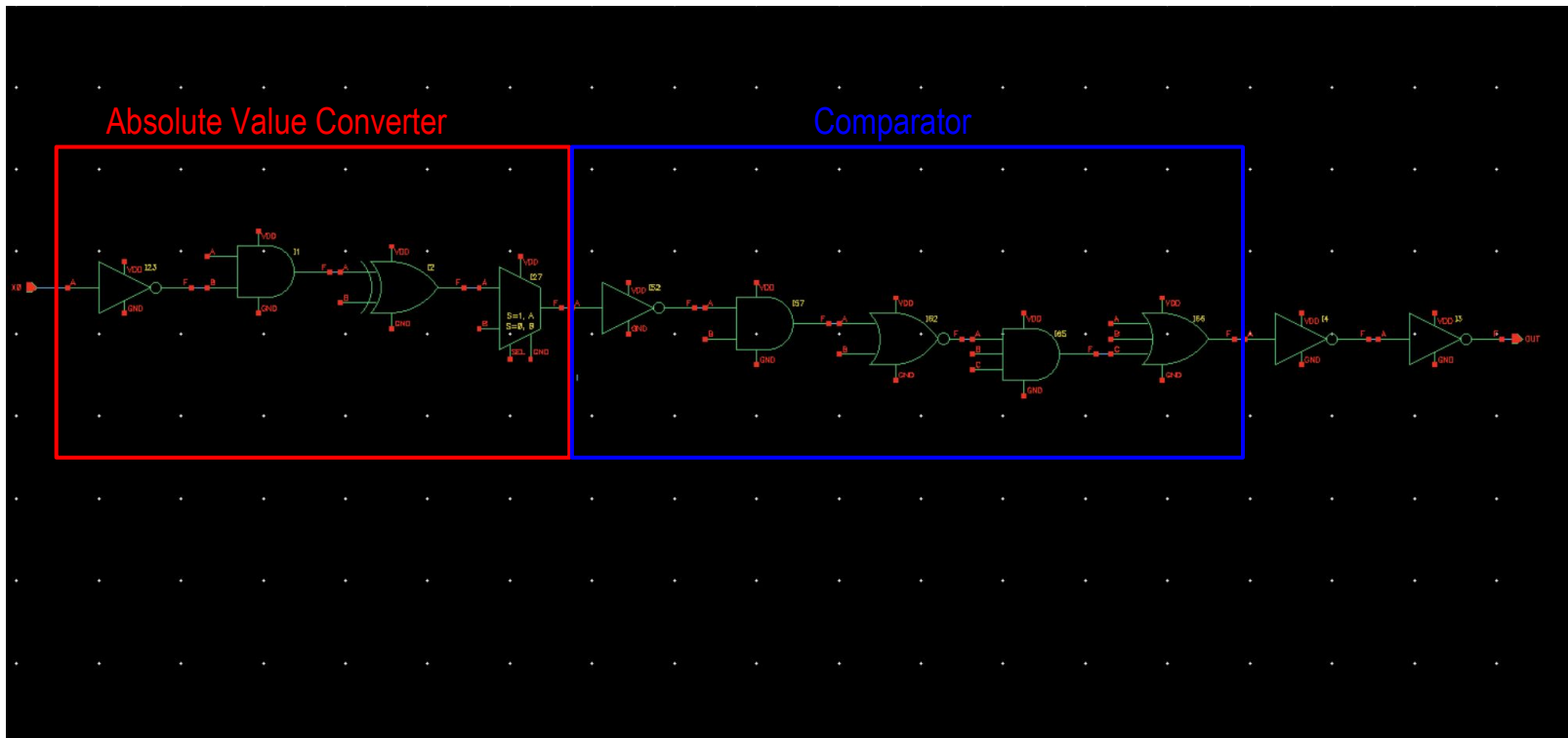

Design Optimization


◆ Gate level critical path

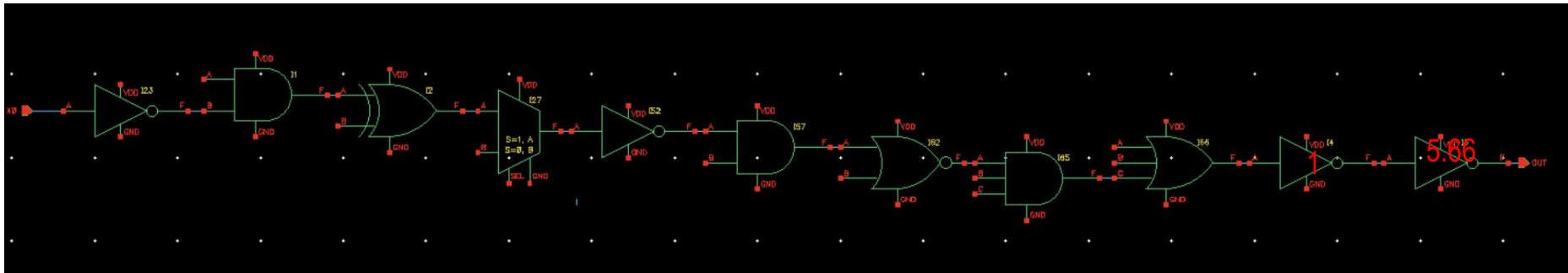


- ◆ MOS detail of gates, optimizations, and sizing strategy
- ◆ Efficient logic design for 2's complement converter without a complex mirror adder structure
- ◆ Pass-transistor logic used for MUX and XOR to reduce overall circuit energy
- ◆ Output buffers used to isolate fan-in from fan-out and improve propagation delay

Functionality Check

 ◆ Relevant waveforms (input to output paths)



Absolute-Value Detector Layout

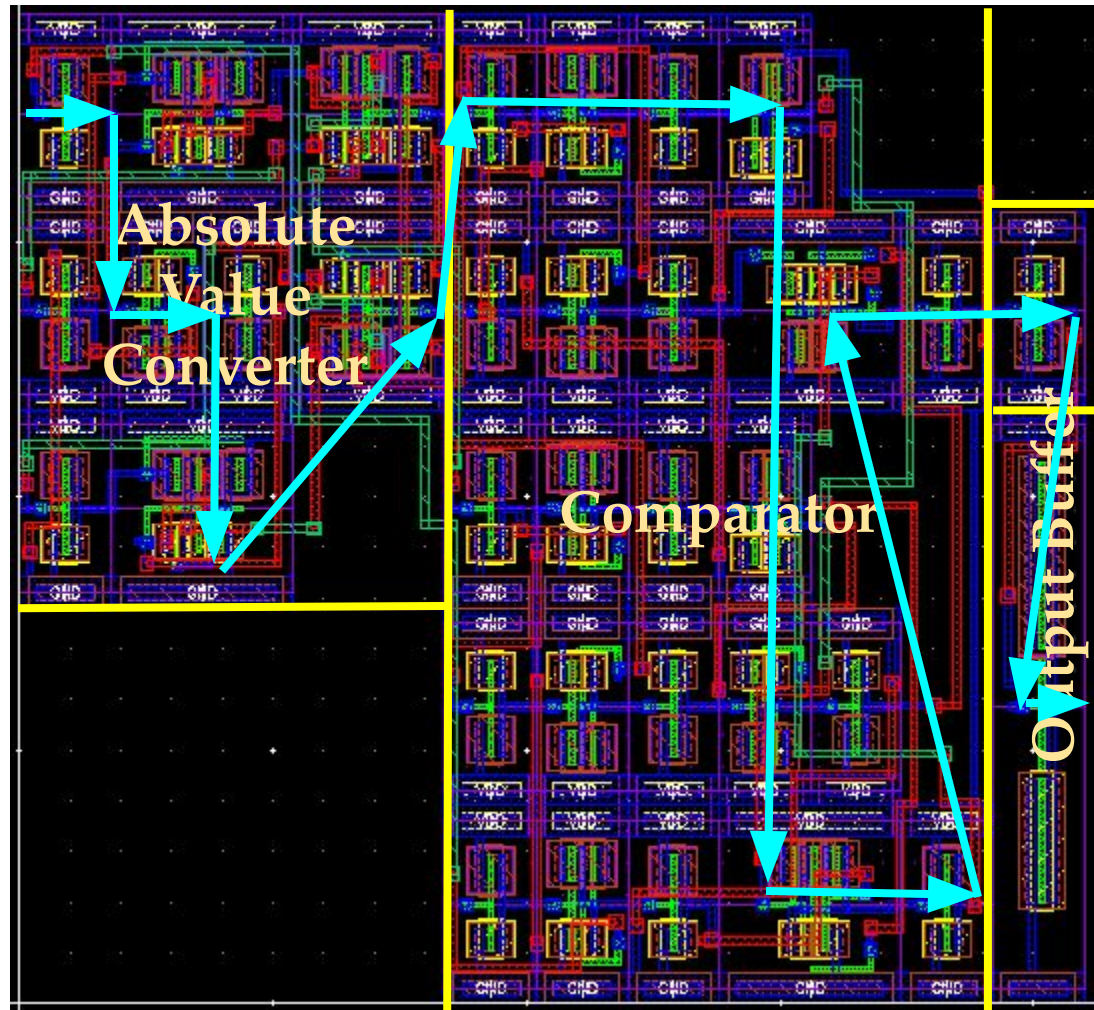

Density
Density:
82.7%

Size
 $Y = 19.5 \mu\text{m}$
 $X = 21 \mu\text{m}$

AR, Area
Aspect ratio:
1.078

Area:
 $409.5 \mu\text{m}^2$

Discussion

◆ **Three most important features of your design**

- Efficient Logic Structure with reduced fan-in for reduced layout area and improved propagation delay
- Isolated Fan-in from Fan-out through the use of Output Buffers
- Usage of pass-transistor logic for reduced power consumption

◆ **Given another chance, 3 things you would do different**

- Improve propagation delay by further sizing analysis
- Optimize critical path by analyzing transistor ordering
- Improve layout design for reduced area and optimized critical path traversal